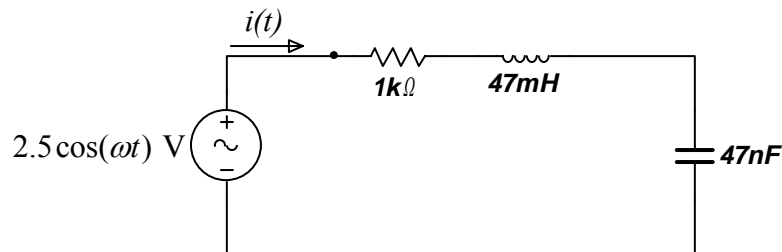


MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
22.071/6.071 Introduction to Electronics, Signals and Measurement  
Spring 2006


*Laboratory 12. Sinusoidal Steady State Response: Impedance.*

Exercise 1.

- a) For the circuit below determine the Thevenin equivalent circuit seen by the 47nF capacitor. Use a frequency of 1000rad/sec.  
The goal here is to become familiar with the impedance method). (consult your notes, work with your partner, ask your instructors for help)




- b) With the additional  $1\text{k}\Omega$  resistor added as indicated below determine the Thevenin equivalent circuit seen by the  $47\text{nF}$  capacitor. The frequency is again  $1000\text{rad/sec}$ .

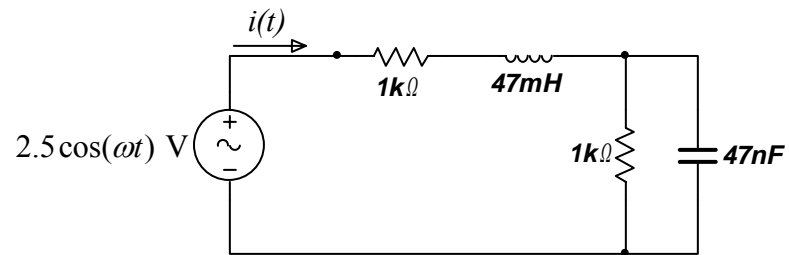

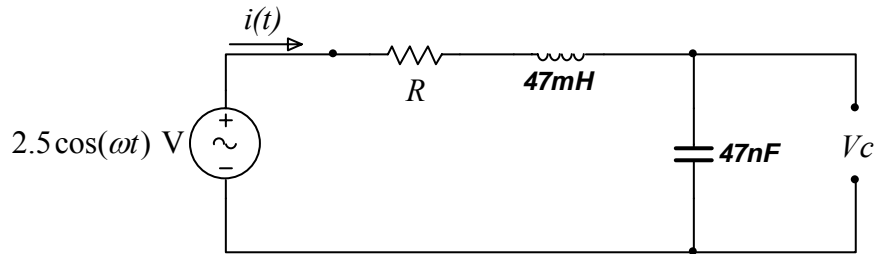Exercise 2.

Now we will measure the voltage  $V_C$  for various combinations of frequency  $\omega$  and  $R$



a) First write the voltage  $V_C$  as a function of  $R$ , and  $\omega$ . (use the voltage divider rule)

b) Now measure the amplitude of  $V_C$  and observe its dependence on  $\omega$ . Use  $R=1.5\text{k}\Omega$ , vary  $\omega$  from  $1,000\text{rad/sec}$  to  $50,000\text{rad/sec}$ . Plot a few values below to show the variation of  $V_C$  with  $\omega$ .




Do your measurements agree with your results from part (a)?

- c) Set the source frequency at 10000rad/sec and vary the value of R and observe the results. Now plot  $V_c$  as a function of R. (a good range of R is from  $100\Omega$  to  $20k\Omega$ )



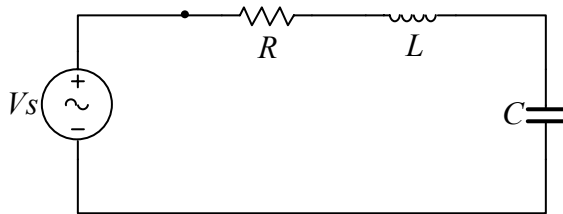- d) (The following two parts for extra credit). Apply Kirchhoff's laws and the voltage current relationships for the elements in the circuit and derive the equation that describes the behavior of this circuit.



- e) Now with  $R=100\Omega$ , apply a square wave pulse signal for  $V_s$  (2.5 Volt magnitude, 500 Hz) and observe the output at one of the transitions. (You will need to adjust the time axis in order to see this effect) How is this different from the case where only a resistor and a capacitor or a resistor and an inductor comprise the circuit? (A simple observation will do)