

MIT 6.772/SMA 5111: COMPOUND SEMICONDUCTOR DEVICES

Problem Set No. 2 Solutions

**Issued:** March 4, 2003

**Due:** March 11, 2003

The values used in this problem set are listed in Table 1.

	$Al_{0.40}Ga_{0.60}As$	$GaAs$
$\chi$ [eV]	3.63	4.07
$E_g$ [eV]	1.92	1.42
$\epsilon_r$	11.6	12.9
$N_C$ [ $cm^{-3}$ ]	$5.0 \times 10^{17}$	$4.7 \times 10^{17}$
$N_V$ [ $cm^{-3}$ ]	$8.0 \times 10^{18}$	$7.0 \times 10^{18}$
$\mu_e$ [ $\frac{cm^2}{V \cdot s}$ ]	600	4000
$\mu_h$ [ $\frac{cm^2}{V \cdot s}$ ]	100	400

Table 1: Values used for this problem set

**Problem 3.1**

 


Figure 1: The MESFET

**Part a: Design a GaAs MESFET:**

The MESFET must be designed such that  $a' = a$  when  $v_{GS} = 0$ .

 


Figure 2: Cross-section of the MESFET.

- $a$ : equilibrium depletion depth.
- $a'$ : Non-equilibrium depletion depth.
- $q\Phi_{bn}$ : Barrier Height.
- $q\Phi_{bi}$ : Built-in Potential.
- $q\Phi'_{bi}$ : Non-Equilibrium Built-in Potential.
- $V_a$ : Applied Voltage.

$$\begin{aligned}
 q\Phi_{bn} &= q\Phi_{bi} + (E_C - E_F) = 0.8 \text{ eV} \\
 E_C - E_F &= \frac{k_B T}{q} \ln \left( \frac{N_C}{N_D} \right) \\
 &= 39.62 \text{ meV} \\
 q\Phi_{bi} &= \frac{q^2}{2\epsilon} N_D a^2 = q\Phi_{bn} - (E_C - E_F) \\
 a' &= \sqrt{\frac{2\epsilon}{q^2 N_D} q\Phi_{bi}} = \sqrt{\frac{2\epsilon}{q^2 N_D} (q\Phi_{bn} - (E_C - E_F))} = 10.41 \times 10^{-6} \text{ cm} \\
 a' &= a = 104.19 \text{ nm}
 \end{aligned}$$

**Part b: What is the maximum conductance, where  $v_{GS} = 0.5 \text{ Volts}$ ?**

 


Figure 3: Position and size of the area in question.

Forward biasing will shrink the depletion depth,  $a'$ . However, the gate is no longer isolated from the

drain/source channel if  $v_{GS} \geq 0.5$  Volts.

$$\begin{aligned}
 q\Phi'_{bi} &= \frac{q^2}{2\epsilon} N_D a^2 = q\Phi_{bn} - (E_C - E_F) - qV_A \\
 a' &= \sqrt{\frac{2\epsilon}{q^2 N_D} q\Phi'_{bi}} = 6.097 \times 10^{-6} \text{ cm} \\
 a - a' &= 4.32 \times 10^{-6} \text{ cm} \\
 \sigma &= qn\mu_e + qp\mu_h \cong qn\mu_e \\
 G &= \sigma \frac{Area}{Length} = \sigma \frac{(a - a') W}{L} = 55.3 \text{ m}\Omega
 \end{aligned}$$

### Part c:

**i: Find the maximum drain current and the corresponding  $v_{DS}$ .**

The maximum drain current occurs when that the carriers are traveling at the saturation velocity.

$$\begin{aligned}
 J &= qns_{sat} = 160 \frac{kAmps}{cm^2} \\
 I &= J \cdot A = J \cdot (a - a') W = 6.91 \text{ mA}
 \end{aligned}$$

If the field is uniform, then Ohm's law should hold.

$$V = \frac{I}{G} = 125 \text{ mV}$$

**ii: Is this assumption valid?**

If  $v_{GS} = 0.5$  V and  $v_{DS} = 125$  mV, then  $v_{GD} = 375$  mV. If we evaluate the depletion on both sides of the device, we will find that the depletion width is deeper on the drain side.

$$\begin{aligned}
 a - a'(V_A = 0.5) &= 43.2 \text{ nm} \\
 a - a'(V_A = 0.375) &= 30.4 \text{ nm}
 \end{aligned}$$

The channel depth was assumed to be uniform when the saturation current and voltage were calculated. The carriers cannot leave the source with the saturation velocity because they must accelerate as they approach the drain (the cross-sectional area decreases as the carriers approach the drain, so the current density (velocity) must increase in order to maintain current continuity).

## Problem 3.2

**Part a: Draw the circuit schematic for a direct-coupled FET logic (DCFL) inverter**

The circuit schematic is shown in Figure 4.

**Part b: Plot the  $v_{in}/v_{out}$  transfer characteristic if the output terminal is open circuited**

First,  $v_{in}$  is limited by metal-semiconductor junction at  $Q_1$ . Thus  $v_{in} \in [0, 0.8]$  Volts. Also there should be 4 regions of operation:

1.  $Q_1$  is in cut off region,  $Q_2$  is in triode region
2.  $Q_1$  is in saturation region,  $Q_2$  is in triode region
3.  $Q_1$  is in saturation region,  $Q_2$  is in saturation region
4.  $Q_1$  is in triode region,  $Q_2$  is in saturation region

 


Figure 4: DCFL Inverter

**Boundaries between regions:**

If  $Q_1$  is in cut off region,  $v_{GS1} \in [0, 0.1]$  Volts and  $I_{D1} = 0$  A. Since  $Q_2$  is in triode region:

$$\begin{aligned} I_{D2} &= K_2 \left( v_{GS2} - V_{P2} - \frac{v_{DS2}}{2} \right) v_{DS2} \\ &= K_2 \left( -V_{P2} - \frac{v_{DD} - v_{out}}{2} \right) (v_{DD} - v_{out}) = 0 \\ v_{out} &= v_{DD} = 2 \text{ Volts} \end{aligned}$$

If  $Q_2$  is in triode region:

$$\begin{aligned} v_{DS2} &< v_{GS2} - V_{P2} \\ v_{DD} - v_{out} &< 0 - (-0.5) \\ v_{out} &> 1.5 \text{ Volts} \end{aligned}$$

If  $Q_1$  is in the saturation region:

$$\begin{aligned} v_{DS1} &> v_{GS1} - V_{P1} \\ V_{out} &> V_{in} - 0.1 \text{ Volts} \end{aligned}$$

**$Q_1$  is in saturation region,  $Q_2$  is in triode region:**

$$\begin{aligned} \frac{K_1}{2} (v_{GS1} - V_{P1})^2 &= K_2 \left( v_{GS2} - V_{P2} - \frac{v_{DS2}}{2} \right) v_{DS2} \\ \frac{K_1}{2} (v_{IN} - V_{P1})^2 &= K_2 \left( -V_{P2} - \frac{v_{DD} - V_{out}}{2} \right) (v_{DD} - V_{out}) \\ 0 &= V_{out}^2 - 3V_{out} + (2.01 + V_{IN}^2 - 0.2V_{IN}) \\ V_{out} &= 1.5 \pm \sqrt{0.24 - V_{IN}^2 - 0.2V_{IN}} \\ \text{In this region, } V_{out} &> 1.5 \text{ Volts} \\ V_{out} &= 1.5 + \sqrt{0.24 - V_{IN}^2 - 0.2V_{IN}} \end{aligned}$$

 


Figure 5: Transfer characteristic of an open circuit DCFL inverter.

**$Q_1$  is in saturation region,  $Q_2$  is in saturation region:**

$$\begin{aligned} \frac{K_1}{2} (v_{GS1} - V_{P1})^2 &= \frac{K_2}{2} (v_{GS2} - V_{P2})^2 \\ (v_{IN} - V_{P1})^2 &= (-V_{P2})^2 \\ V_{in} &= V_{P1} - V_{P2} \\ V_{in} &= 0.6 \text{ Volts} \end{aligned}$$

**$Q_1$  is in triode region,  $Q_2$  is in saturation region:**

$$\begin{aligned} \frac{K_2}{2} (v_{GS2} - V_{P2})^2 &= K_1 \left( v_{GS1} - V_{P1} - \frac{v_{DS1}}{2} \right) v_{DS1} \\ (-V_{P2})^2 &= 2 \left( V_{in} - V_{P1} - \frac{V_{out}}{2} \right) V_{out} \\ 0 &= V_{out}^2 - (0.2 - 2V_{in}) V_{out} + 0.25 \\ V_{out} &= (V_{in} - 0.1) \pm \sqrt{V_{IN}^2 - 0.2V_{IN} - 0.24} \\ \text{In this region, } V_{out} &< V_{in} - V_{P1} \\ V_{out} &= (V_{in} - 0.1) - \sqrt{V_{IN}^2 - 0.2V_{IN} - 0.24} \end{aligned}$$

**Part c: Plot the  $v_{in}/v_{out}$  transfer characteristic if the output terminal is connected to another DCFL inverter.**

The input terminal of the next terminal is essentially a metal-semiconductor junction. If  $V_{in} > 0.8 \text{ Volts}$ , then the output of the first inverter is pinned at 0.8 volts, as shown in Figure 6. If the output is less than 0.8 volts, the transfer curve should be the same as the previous case.

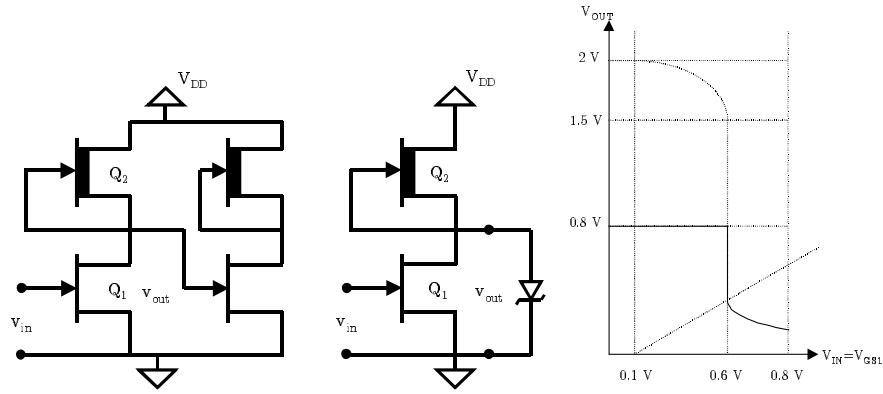


Figure 6:

### Problem 3.3

Part a: Calculate the emitter defect of the HBT

$$\begin{aligned}
 \delta_E &= \frac{J_h}{J_e} \\
 J_e &= q \frac{n_{po} D_{e,B}}{w_B} \left( e^{-\frac{qV}{k_B T}} - 1 \right) \\
 n_{po} &= \frac{n_{i,base}^2}{N_{A,B}} = \frac{N_{C,B} N_{V,B} e^{-\frac{E_{g,B}}{k_B T}}}{N_{A,B}} \\
 J_h &= q \frac{p_{no} D_{h,E}}{w_e} \left( e^{-\frac{qV}{k_B T}} - 1 \right) \\
 p_{no} &= \frac{n_{i,emitter}^2}{N_{D,E}} = \frac{N_{C,E} N_{V,E} e^{-\frac{E_{g,E}}{k_B T}}}{N_{D,E}} \\
 \delta_E &= \frac{w_B D_{h,E} N_{A,B}}{w_E D_{e,B} N_{D,E}} \frac{N_{C,B} N_{V,B}}{N_{C,E} N_{V,E}} e^{-\frac{E_{g,E} - E_{g,B}}{k_B T}} \\
 &= 9.69 \times 10^{-8}
 \end{aligned}$$

Part b: Calculate the sheet resistance of the base region

$$\begin{aligned}
 R_{\square} &= \frac{\rho}{t} = \frac{1}{\sigma \cdot w_B} \\
 &= \frac{1}{q \mu_{h,B} N_{A,B} w_B} \\
 &= 312.5 \frac{\Omega}{\text{square}}
 \end{aligned}$$

**Part c: Calculate the depletion capacitance between the collector/base junction.**

$$\begin{aligned}\phi_{bi,BC} &= k_B T \cdot \ln \left( \frac{N_{A,B} N_{D,C}}{n_{i,B}^2} \right) = 1.371 \text{ eV} \\ x_{D,B} &= \sqrt{\frac{2N_{D,C}\epsilon_B (\phi_{bi} - qV_A)}{q^2 N_{A,B} (N_{A,B} + N_{D,C})}} = 1.546 \text{ nm} \\ x_{D,C} &= \frac{N_{A,B}}{N_{D,C}} x_{D,B} = 309.285 \text{ nm} \\ C' &= \frac{\epsilon_B}{w_D} = \frac{\epsilon_B}{x_{D,B} + x_{D,C}} = 36.75 \frac{\text{nF}}{\text{cm}^2}\end{aligned}$$

**Part d: Calculate the base transit time.**

$$\tau = \frac{w_B^2}{2D_{e,B}} = 122.07 \text{ fs}$$